

Tutorial Arithmetic

Shreyas Dodamani
19114079

1) $(-5) \times (-7)$

Iterative: Convert -5 and -7 to positive numbers, multiply them, the negative if initial signs contrast.

5x7:		(initially)		
C	A	Q	M	
0	0000	0101	0111	Initial values
0	0111	0101	0111	$A = A + M$ } ①
0	0011	1010	0111	Shift
0	0001	1101	0111	Shift } ②
0	0000	1100	0111	$A = A + M$ } ③
0	0100	0110	0111	Shift
0	0010	0011	0111	Shift } ④

AQ: 00100011 = 35 = 5x7

Since signs of -5 & -7 match, don't negative
 $-5 \times -7 = 35$

BOOTH'S: -5

A	Q	Q ₋₁	M	
0000	1011	0	1001	Initial values
0111	1011	0	1001	$A = A + (-M)$ } $Q_0 Q_{-1} = 10$
0011	1101	1	1001	Shift
0001	1110	1	1001	Shift } $Q_0 Q_{-1} = 11$
1010	1110	1	1001	$A = A + M$ } $Q_0 Q_{-1} = 01$
1101	0111	0	1001	Shift
0100	0111	0	1001	$A = A - M = A + (-M)$ } $Q_0 Q_{-1} = 10$
0010	0011	1	1001	Shift


\Rightarrow ANSWER = AQ = 00100011 = (35)

$(-5) \times (-7) = 35$

2) Multiplicand: 0101 1010 1110 1110
Multiplier: 0111 0111 1011 1101

Multiplier

Q₋₁

 

Every time we encounter 01: ADD
10: SUBTRACT

⇒ 4 ADD operations
4 SUBTRACT operations



8 TOTAL

- 3) (A) 101010...1010 ⇒ we must perform and add or subtract operation on every step. b/c every step has either 10 or 01
- (B) 1000...001 ⇒ one add and one subtract operation at ~~start~~ initial cycle & final cycle.
- (C) 111...111 ⇒ NO ADD/SUBTRACT operations b/c always 11
- (D) 0111...1110 ⇒ one subtract operation in beginning and one at end.
→ 2 OPERATIONS

calculations done while ignoring initial 0 value of Q₋₁ b/c it adds to each option by same amount


SINCE (A) is most computationally expensive, Booth's algorithm has least performance

4) Full Adder

  


⇒ 7 AND
2 OR

Half Adder

 

⇒ 3 AND
1 OR

④ Ripple Carry Adder

 

We require 3 full adders and 1 Half adder

In 1 full adder, we have

7 AND gates

2 OR gates

$$\Rightarrow \begin{array}{l} 3(7) \\ \text{AND} \\ \text{GATES} \end{array} + \begin{array}{l} 3(2) \\ \text{OR} \\ \text{GATES} \end{array} = \begin{array}{l} 21 \text{ and} \\ \text{gates} \end{array} + \begin{array}{l} 6 \text{ OR} \\ \text{gates} \end{array}$$

In 1 half adder we have


3 AND gates

1 OR gate

$$\begin{array}{l} \text{total:} \\ (3 + 21) = 24 \text{ AND gates} \\ (6 + 1) = 7 \text{ OR gates} \end{array}$$



Carry select adder.

given $n=4 \Rightarrow k=\sqrt{4}=2$

 


$$\begin{matrix} A_4 & A_3 & A_2 & A_1 \\ B_4 & B_3 & B_2 & B_1 \end{matrix}$$

Block:

  

 FOR one FA: 2 OR gates, 7 AND gates.
 $\Rightarrow 4 \text{ FA} = 4(2 \text{ OR} + 7 \text{ AND})$
 $= \boxed{8 \text{ OR} + 28 \text{ AND}}$



1 selector $\Rightarrow 2 \text{ AND} + 1 \text{ OR}$
 $\Rightarrow 3(2 \text{ AND} + 1 \text{ OR})$
 $= 6 \text{ AND} + 3 \text{ OR}$

} 3 selectors because
 $\frac{x2 \times 1}{3}$

\Rightarrow In one block: $(6+28) \text{ AND} + (3+8) \text{ OR}$
 $= (34) \text{ AND} + (11) \text{ OR}$

Since there are 2 blocks,
 $2 (34 \text{ AND} + 11 \text{ OR})$
 $= 68 \text{ AND and } 22 \text{ OR gates}$
 for carry select adder

Carry Lookahead adder

To calculate C_i :

$$C_0 = 0$$

$$C_1 = C_0 P_0 + G_0 = G_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0)$$


$$= G_2 + P_2 G_1 + P_2 P_1 G_0$$

$$C_4 = G_3 + P_3 (C_3) = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0) = G_3 + P_2 P_1 P_3 G_0$$

$$+ P_3 G_2 + P_3 P_2 G_1$$

FOR $C_0 \Rightarrow 0$ Gates

$C_1 \Rightarrow G_0$ (0 Gates)

 

$$C_3 \Rightarrow G_2 + \underbrace{P_1 G_1}_{1 \text{ AND}} + \underbrace{P_2 P_1 G_0}_{2 \text{ AND}}$$

2 OR GATES

$$C_4 \Rightarrow G_3 + \underbrace{P_2 P_1 P_3 G_0}_{3 \text{ AND}} + \underbrace{P_3 P_2 G_1}_{2 \text{ AND}} + \underbrace{P_3 G_2}_{1 \text{ AND}}$$

3 OR

$$\text{TOTAL} = (1 + 3 + 6) \text{ AND } \& (1 + 2 + 3) \text{ OR GATES}$$

$$= 10 \text{ and } \& 6 \text{ OR gates}$$

To calculate values of C .

FOR $P_i \neq G_i$:

$$P_i = A_i \oplus B_i = \underbrace{A_i \bar{B}_i + \bar{A}_i B_i}_{2 \text{ AND, 1 OR}}$$

$$G_i = \underbrace{A_i B_i}_{1 \text{ AND}}$$

$$\begin{aligned} 4 \text{ bits} &\Rightarrow 4(2 \text{ AND} + 1 \text{ OR}) + 4(1 \text{ AND}) \\ &= 8 \text{ AND} + 4 \text{ AND} + 4 \text{ OR} \\ &= 12 \text{ AND} + 4 \text{ OR} \end{aligned}$$

$$S_i: S_i = C_i (A_i \oplus B_i)$$

$$\text{For } S_0: C_0 = 0 \Rightarrow S_0 = A_0 \oplus B_0 \Rightarrow \underline{2 \text{ AND}}, 1 \text{ OR}$$

$$S_{1,2,3}: S_i = C_i (A_i \oplus B_i) = 3 \text{ AND}, 1 \text{ OR}$$

$$\Rightarrow 3(3 \text{ AND} + 1 \text{ OR}) = 9 \text{ AND} + 3 \text{ OR}$$

$$\Rightarrow (9 + 2) \text{ AND} + (1 + 3) \text{ OR} = 11 \text{ AND} + 4 \text{ OR}$$

$$\begin{aligned} \text{TOTAL} &= (11 + 12 + 10) \text{ AND} + (4 + 4 + 6) \text{ OR} \\ &= 33 \text{ AND} + 14 \text{ OR} \end{aligned}$$

5) complexity = $O(n) \times O(\text{complexity of addition})$

if we use carry look ahead adder,

Complexity of addition = $O(\log n)$

$\Rightarrow O(n \log n)$ = complexity of
Booth's algorithm

if we use ripple carry,

Complex of addition = $O(n^2)$

\Rightarrow complexity of
Booth's algorithm = $O(n^2)$

Booth's Algorithm

- No need to negate values for negative operands
 - complexity same for
 - for cases like
111111...
- Booth's is faster

Iterative Algorithm

- Negative numbers need to be negated
- both algorithms is same
- for cases like
101010...
- Iterative is faster.