

Name: Sharshank Aital

Em. No: 19114076

Batch 04

Branch: CSE

Q.1

$$n=4, \quad M = (-7) \quad ; \quad Q = (-5)$$

$$= (1001)_2 \quad \quad \quad = (1011)_2$$

$$-M = (0111)_2 \quad \quad \quad -M = (0101)_2$$

Iterative procedure-

$$7 \times 5 \Rightarrow \begin{array}{r} & 0 & 1 & 1 & 1 \\ \times & 0 & 1 & 0 & 1 \\ \hline & 0 & 1 & 1 & 1 \\ + & 0 & 0 & 0 & 0 \\ + & 0 & 1 & 1 & 1 \\ + & 0 & 0 & 0 & 0 \\ \hline 0 & 1 & 0 & 0 & 0 & 1 & 1 \end{array} (= 35)$$

∴ Both signs are same, don't negate
 $\Rightarrow (-7) \times (-5) = (35) = \underline{\underline{(0100011)_2}}$

Booth's Algorithm:

n	A	Q	q_{-1}	Comment
4	0000	1011	0	Initialize
3	0111	1011	0	$10 \Rightarrow A-M$
2	0011	1101	1	Right shift ; $n \rightarrow n-1$
1	0011	1110	1	$11 \Rightarrow$ Right shift ; $n \rightarrow n-1$
0	1010	0111	0	$01 \Rightarrow A+M$
	0100	0111	0	$10 \Rightarrow A-M$
	0010	0011	1	Right shift ; $n \rightarrow n-1$

Ans: $AQ = (00100011)_2 = \underline{\underline{(35)_10}}$

Terminate

Q.2. Given: Multiplicand, (M) = 0101 1010 1110 1110

Multiplicand, (Q) = 0111 0111 1011 1101

Append a trailing '0' to multiplicand ($q_0 q_1$)
Booth's code (comparisons) are,

01	\rightarrow Add	
11	\rightarrow X	
11	\rightarrow X	
10	\rightarrow Sub	\Rightarrow 4 Additions
01	\rightarrow Add	
11	\rightarrow X	\Rightarrow 4 subtractions
11	\rightarrow X	
11	\rightarrow X	
10	\rightarrow Sub	
01	\rightarrow Add	
11	\rightarrow X	
11	\rightarrow X	
11	\rightarrow X	
10	\rightarrow Sub	
01	\rightarrow Add	
10	\rightarrow Sub	

Q.3. Booth's algorithm adds/subtracts only when $q_0 q_1$ are 01 or 10.

\Rightarrow Worst case performance occurs when 01 or 10 occur frequently i.e. 1 & 0 alternate.

\Rightarrow Option(A): 101010...1010 gives worst case performance

Q.4.(i) Ripple Carry Adder-

Consists of 3 Full Adders & 1 Half Adder.

In 1 Full adder \Rightarrow 7 AND Gates
2 OR Gates

In 1 Half adder \Rightarrow 2 AND Gates
1 OR Gate

$$\Rightarrow \text{Total ANDs} = 7 \times 3 + 2 = \underline{\underline{23}}$$

$$\Rightarrow \text{Total ORs} = 2 \times 3 + 1 = \underline{\underline{7}}$$

(II) Carry Look Ahead Adder

~~→ We use generator & propagator functions.~~

~~→ For C_i ,~~

~~$\text{no. of AND Gates} = 6$~~

~~$\text{no. of OR gates} = 3$~~

~~→ For P_i ,~~

~~$\text{no. of AND gates} = 8$~~

~~$\text{no. of OR gates} = 4$~~

~~→ For G_i ,~~


~~$\text{no. of AND gates} = 4$~~

~~$\Rightarrow \text{For } S_i, \text{ no. of AND gates} = 8 + 8 + 6 + 4 = \underline{\underline{26}}.$~~


~~$\text{no. of OR gates} = 4 + 4 + 3 = \underline{\underline{11}}.$~~

~~• Circuits used in Q4:~~


~~Half Adder:~~

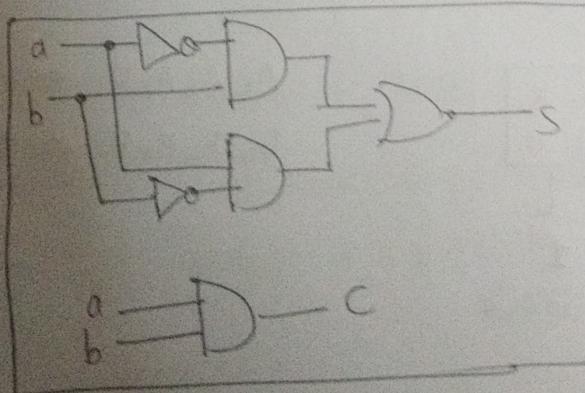

~~Optimized:~~

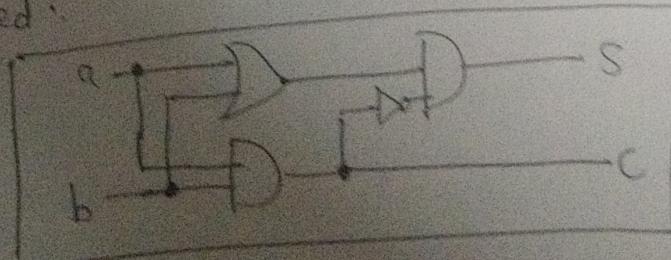


Full Adder:

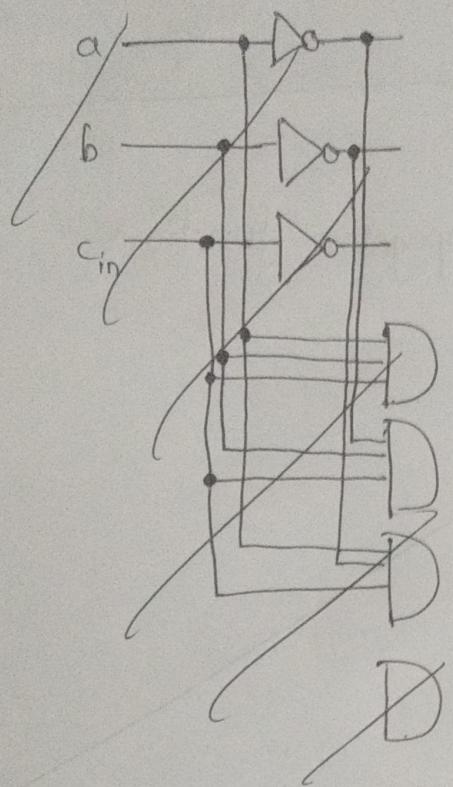


$$S = A \oplus B \oplus C$$

$$\text{Carry} = AB + BC + CA$$

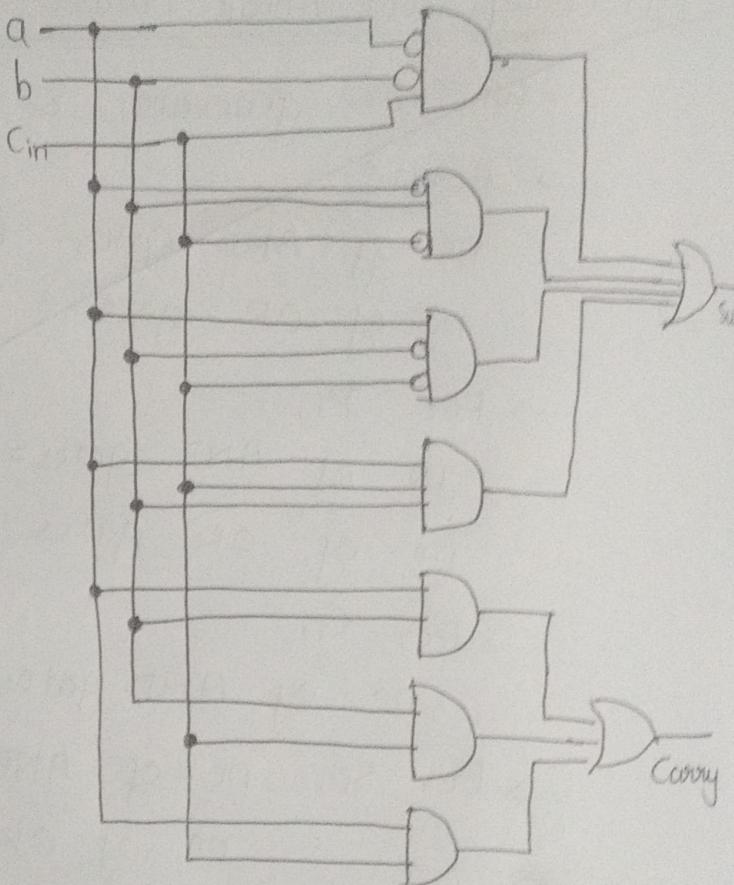


(II) Carry Select Adder-

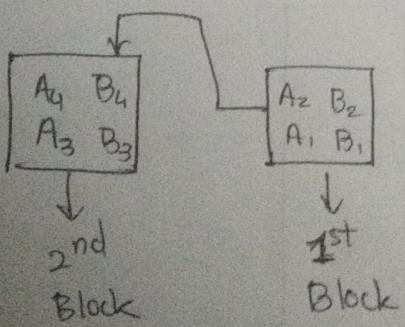

$A_4 A_3 A_2 A_1 \leftarrow 1^{\text{st}}$ number
 $B_4 B_3 B_2 B_1 \leftarrow 2^{\text{nd}}$ number


Block:

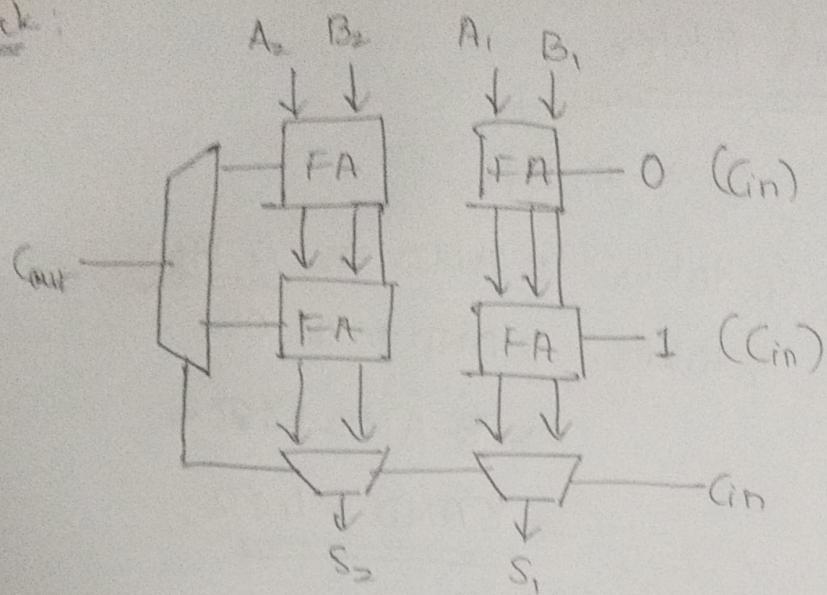

1 FA \Rightarrow 7 AND + 2 OR gates

\Rightarrow 4 FA's \Rightarrow 28 AND + 8 OR gates

For MUX:

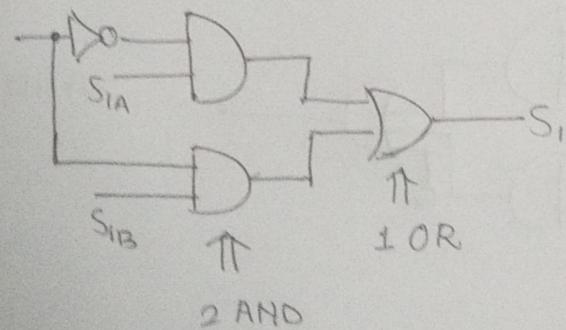

3 selector \Rightarrow (2 AND + 1 OR) \times 3

\Rightarrow 6 AND + 3 OR

\Rightarrow 1 block \Rightarrow (6+20) AND + (3+8) OR

$$= 34 \text{ AND} + 11 \text{ OR}$$

(III) Carry Look Ahead Adder -

$$P_i = A_i \oplus B_i \quad G_i = A_i \cdot B_i$$


For every bit G_i takes 1 AND \Rightarrow 4 AND

For every bit, P_i takes 2 AND + 1 OR

\Rightarrow 8 AND + 4 OR


= 8 AND + 4 OR

$$G_1 \Rightarrow$$

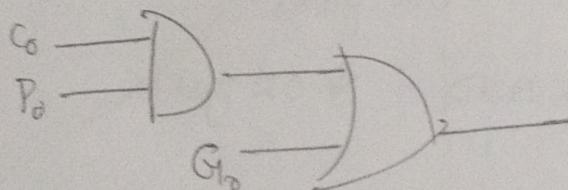


1 AND + 1 OR

$$G_2 \Rightarrow$$

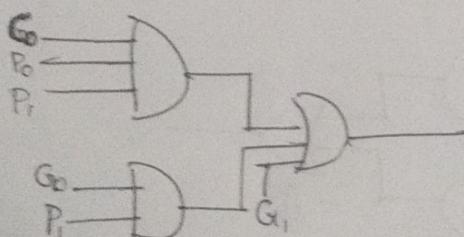

2 AND + 1 OR

$$G_3 \Rightarrow$$

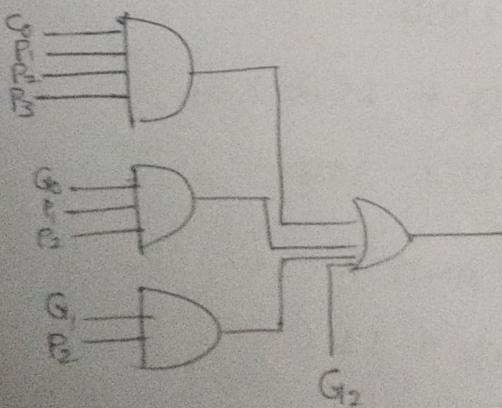

3 AND + 1 OR

Similarly, for $G_4 \Rightarrow$ 4 AND + 1 OR

Now, $S = C_{in} [A \oplus B] \Rightarrow 8 \text{ AND } \& 4 \text{ OR Gates}$

$\Rightarrow \text{Total AND gates: } 4 + 8 + (1+2+3+4) + 8 = \cancel{27 \text{ Gates}} \underline{30 \text{ gates}}$

$\Rightarrow \text{Total OR gates: } 4 + 4 + 4 = \underline{12 \text{ Gates.}}$

Q. 5. We add/subtract in Booth's Algorithm when we encounter $q_0 q_{-1} = 10$ or 01 .

Now, if there are n bits \Rightarrow these sums can be for n B times

\Rightarrow Complexity = $O(n \log n)$ if we use carry look ahead adders.

\Rightarrow Now, iterative process is slower than Booth's algorithm for numbers in 2's compliment form as it involves converting a number between its 2's compliment form.